

线性应用:


$$u_P = u_N, \quad i_N = i_P = 0, \quad \text{负反馈}$$

非线性应用:


$$u_O \begin{cases} +U_{max} \rightarrow u_P > u_N \\ -U_{max} \rightarrow u_P < u_N \end{cases}$$


$$i_P = i_N = 0$$

● 积分器

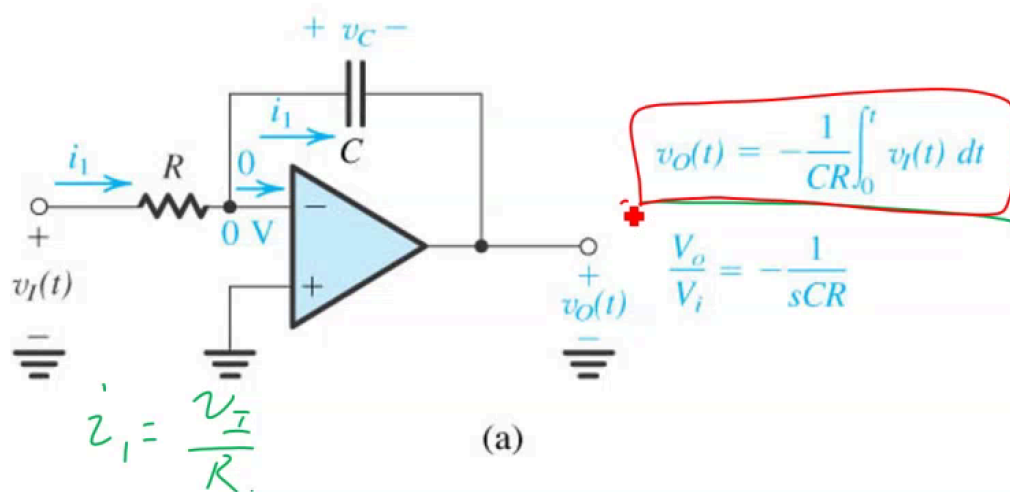

The Miller or inverting integrator.

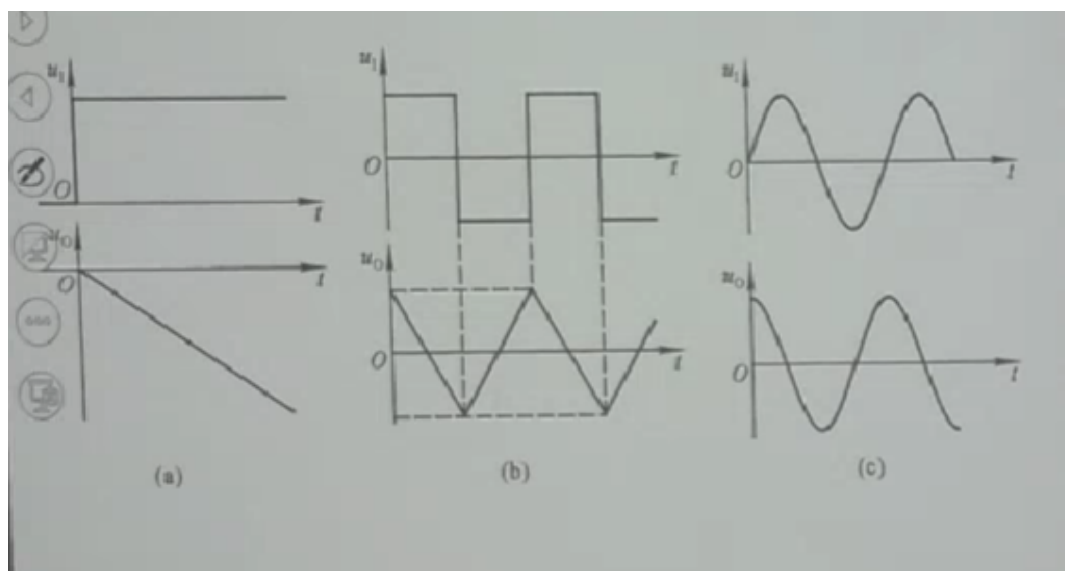


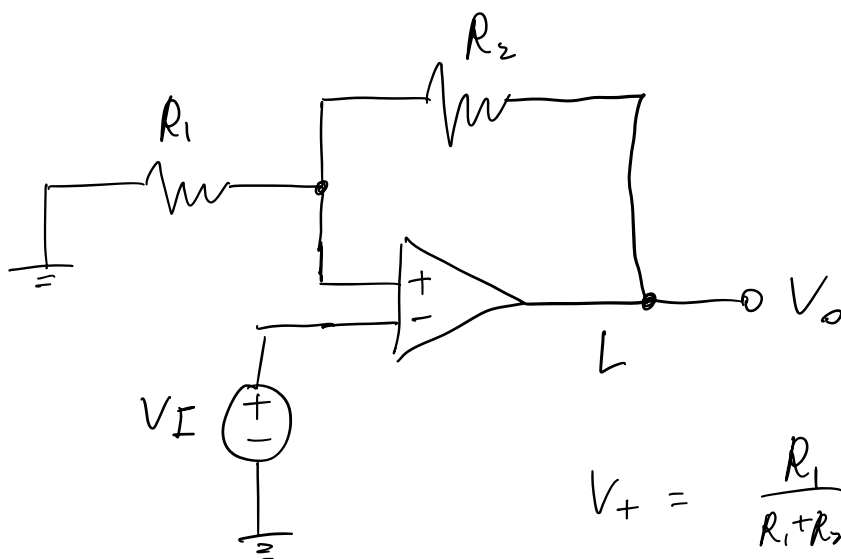


$$V_+ = \frac{R_1}{R_1 + R_2} L = \beta L$$

当 $L = L_+ > 0$,

当 $L = L_- < 0$

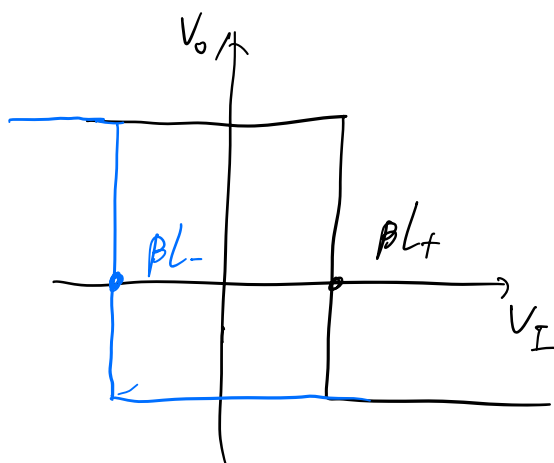


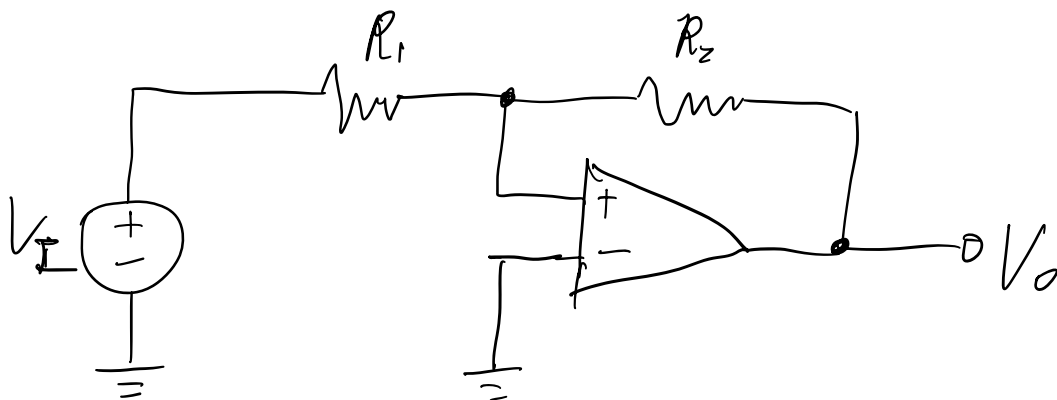


$$V_+ = V_I \frac{R_2}{R_1 + R_2} + V_0 \frac{R_1}{R_1 + R_2}$$

$$V_I \frac{R_2}{R_1 + R_2} + L_+ \frac{R_1}{R_1 + R_2}$$
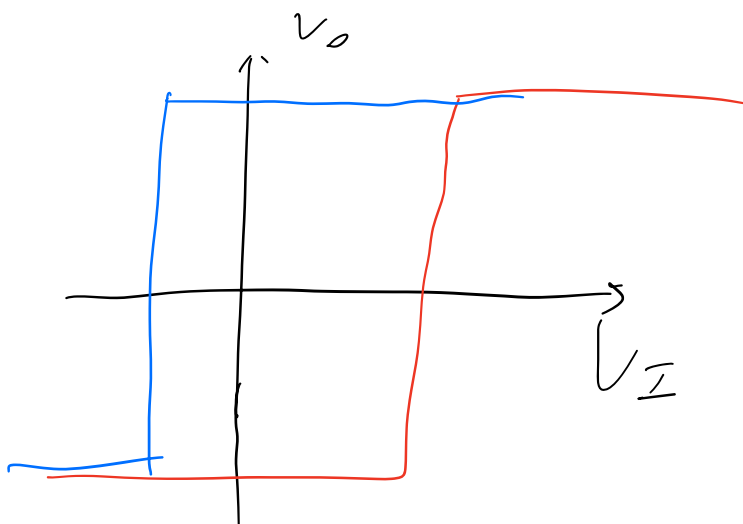
$$V_I \frac{R_2}{R_1 + R_2} + L_- \frac{R_1}{R_1 + R_2}$$





● 反馈

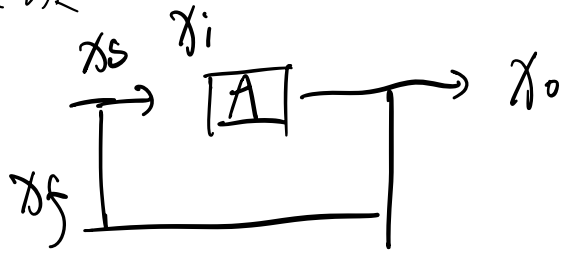

$$x_i = x_s$$

$$x_i = x_s + x_f \quad \text{正}$$

$$= x_s - x_f \quad \text{负}$$

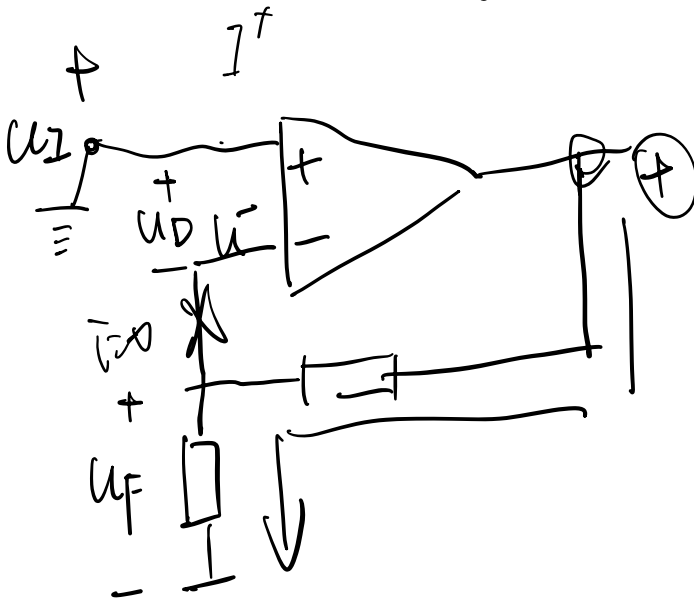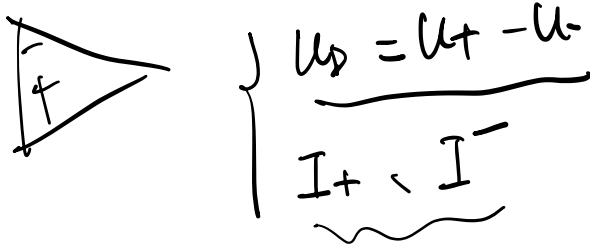

$$u_I = u_o + u_F$$

$$u_o = u_I - u_F \quad \text{负}$$