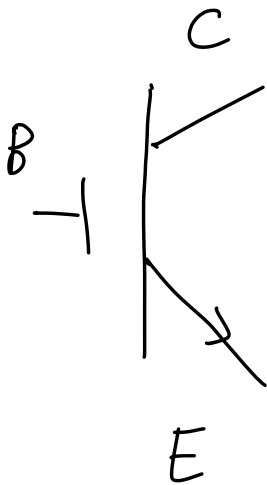


● $i_C = \bar{I}_s e^{V_{BE}/V_T}$

● $i_E = i_B + i_C$

$i_C = \beta i_B$



DC 分析:

① $V_{BE} = 0.7V$, 若 $V_{BE} < 0.7V$
不工作

$i_B = i_C = i_E = 0$

②

1° $V_C > V_B$


$i_C = \beta i_B$

2° $V_C < V_B$

$V_{CE} = 0.2V$

$$i_c \neq \beta i_B$$

戴维南等效

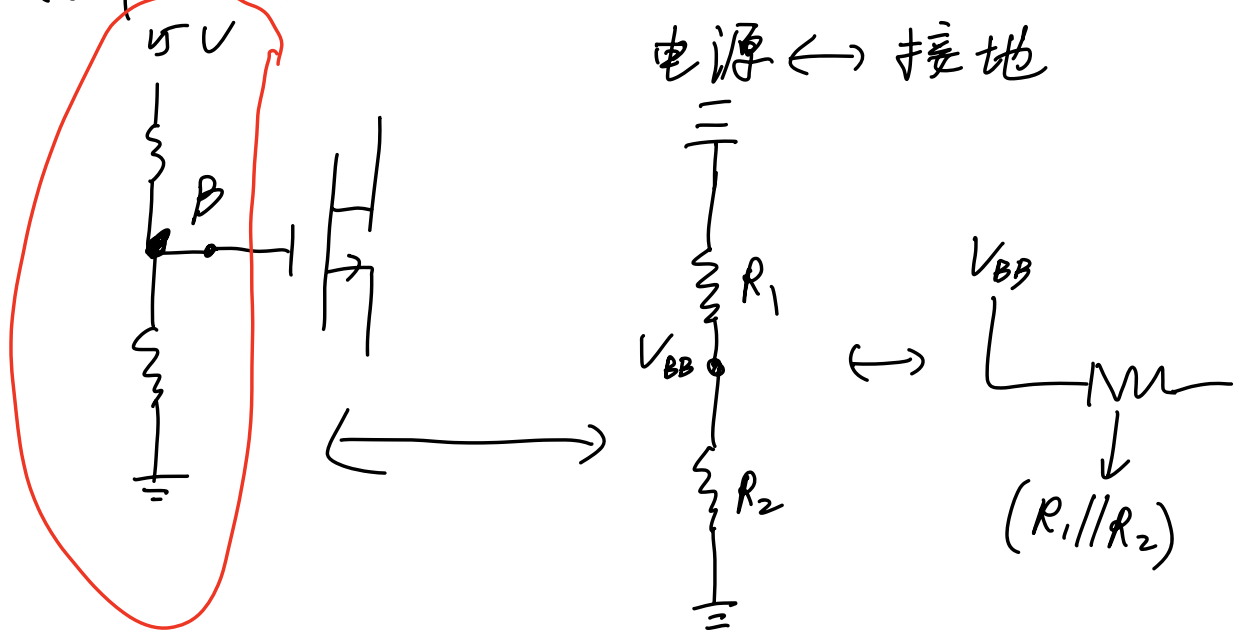

$$V_{BB} = \frac{R_2}{R_1 + R_2} \cdot 15V$$

小信号模型

$$\begin{aligned}
 I_c + i_c &= I_s e^{(V_{BE} + v_{be})/V_T} \\
 &= \hat{I}_s e^{V_{BE}/V_T} \cdot e^{v_{be}/V_T} \\
 &= I_c e^{v_{be}/V_T} \\
 &= I_c \left(1 + \frac{v_{be}}{V_T} \right)
 \end{aligned}$$


$$\Rightarrow i_c = \frac{I_C V_{be}}{V_T} = g_m V_{be}$$

● 混合 π 模型 (E 直接接地)

i_b

i_c


$$V_T = 0.025$$

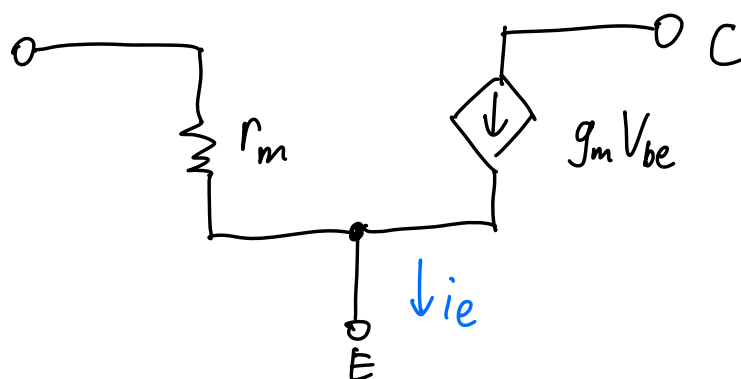

$$g_m = I_C / V_T$$


$$r_m = \beta / g_m$$

不理想:

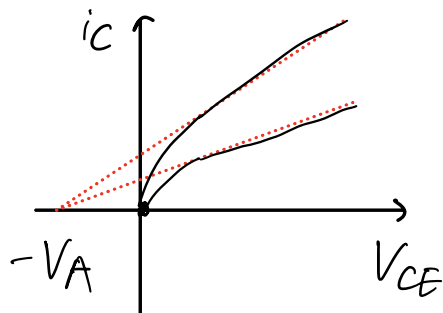


$$i_c = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A} \right)$$
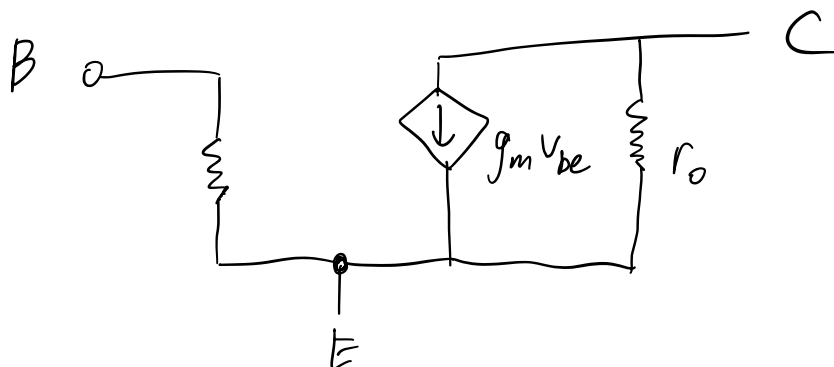
$$r_o = \left(\frac{\partial i_c}{\partial V_{CE}} \right)^{-1} = \frac{V_A}{I_C}$$




● T 模型 (E 极接了电阻)


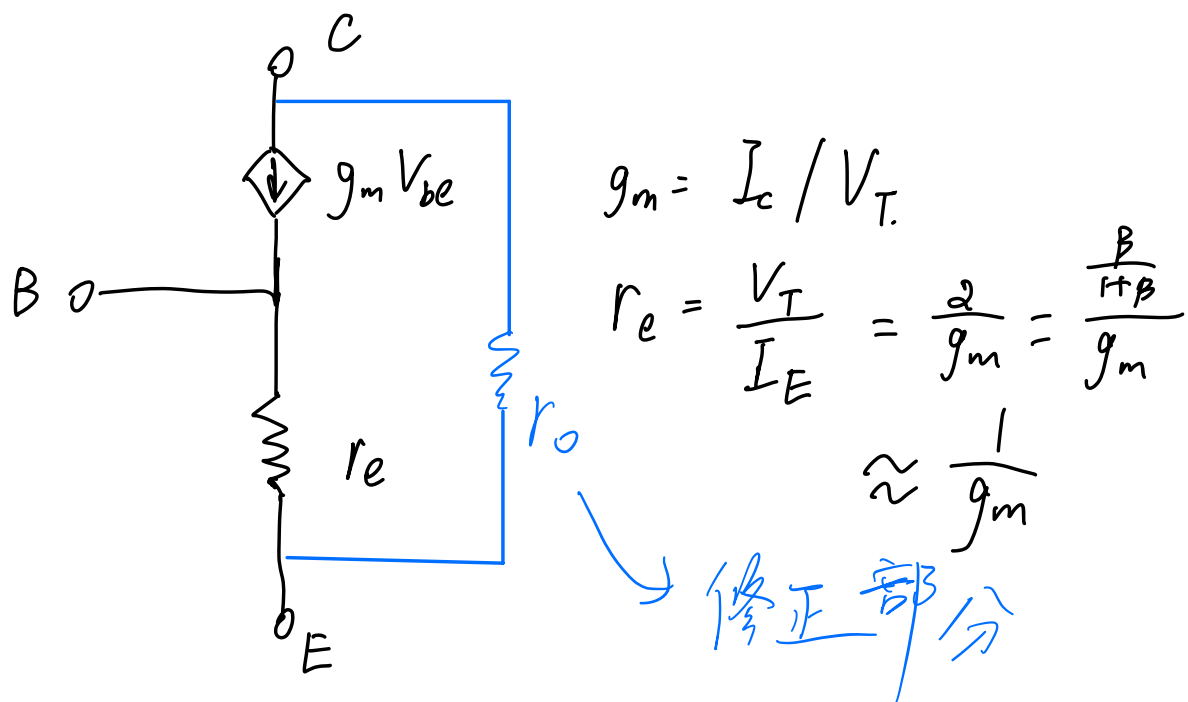


● 交流分析

先求直流

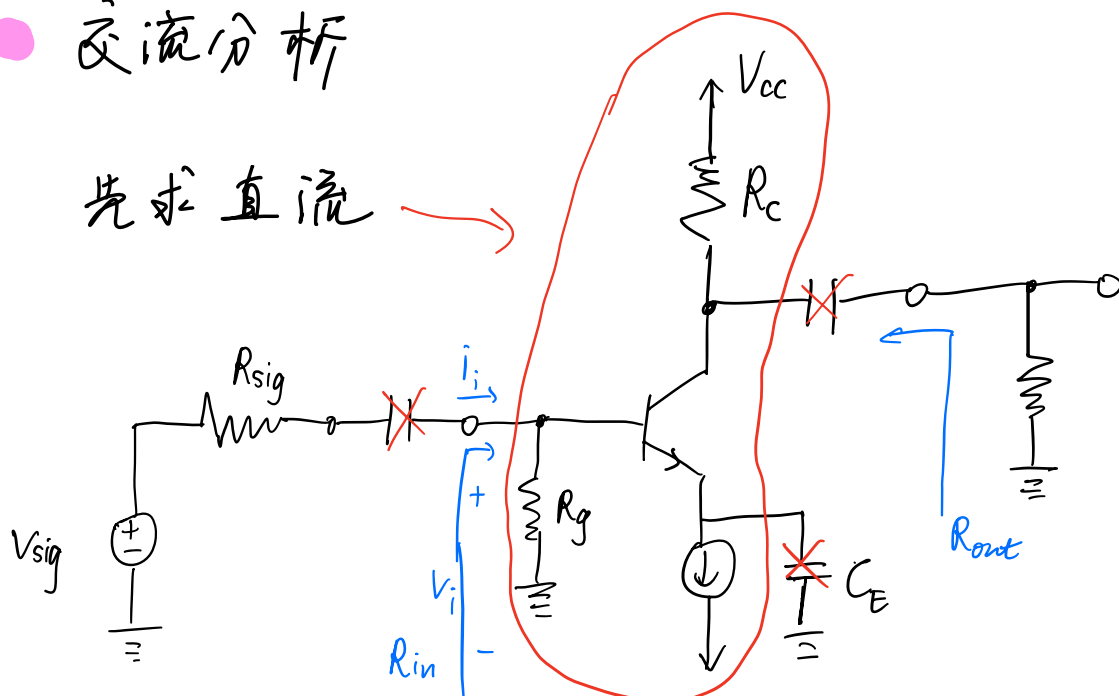

② 化简交流电路

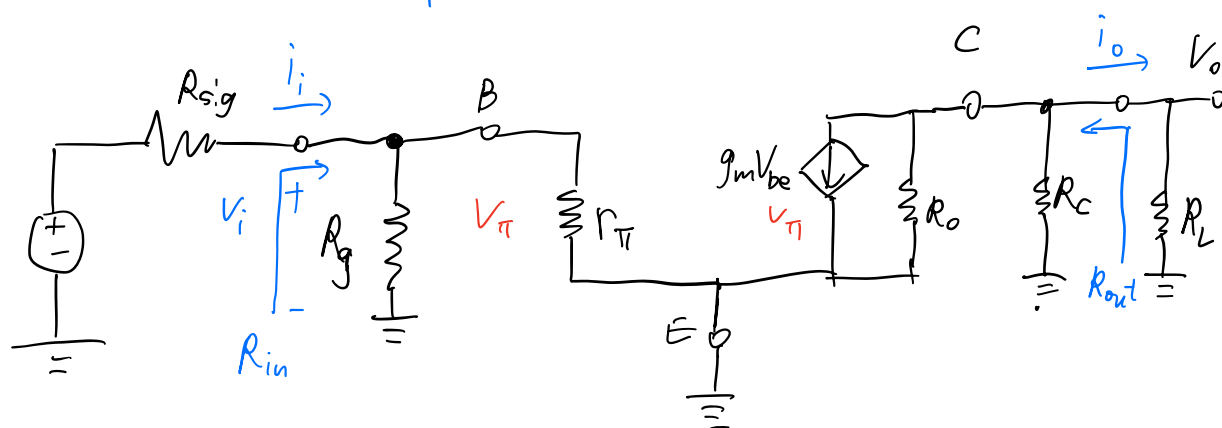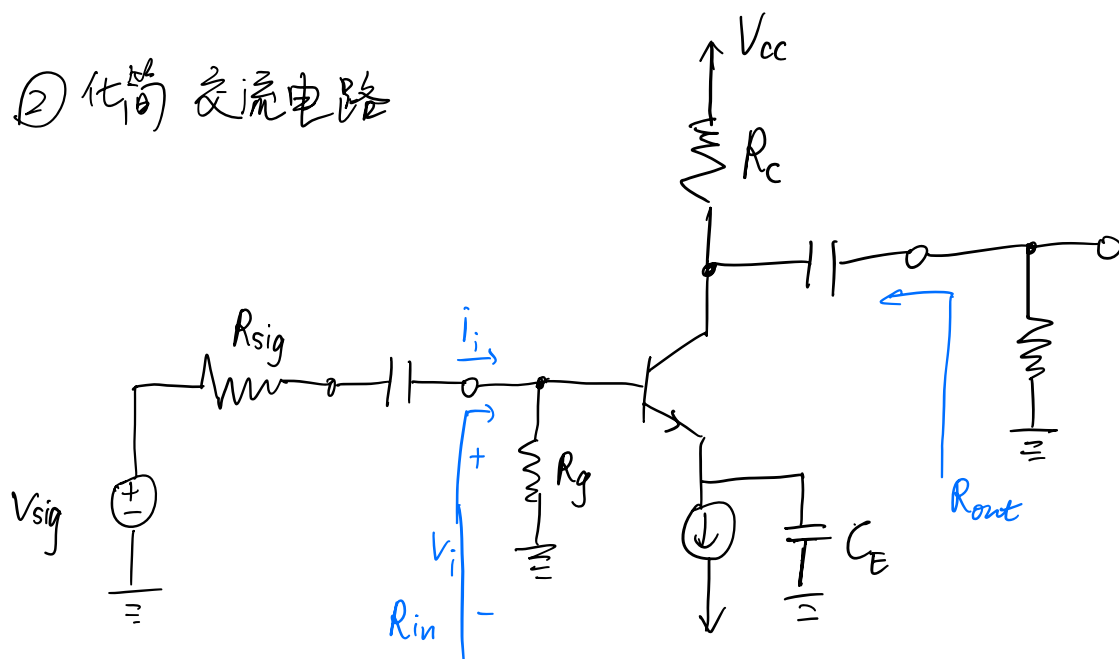

$$R_{in} = \frac{V_i}{i_i} = (R_g \parallel r_{\pi})$$


$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{\pi} (R_o \parallel R_c \parallel R_L)}{V_{\pi}} \quad (\text{负号同方向})$$

$$R_{out} = (R_o \parallel R_c) \approx R_c$$


$$G_V = \frac{V_o}{V_{sig}} = A_v \cdot \frac{R_{in}}{R_{in} + R_{sig}}$$

$$\frac{V_o}{V_i} \cdot \frac{V_i}{V_{sig}}$$

● 共射放大电路

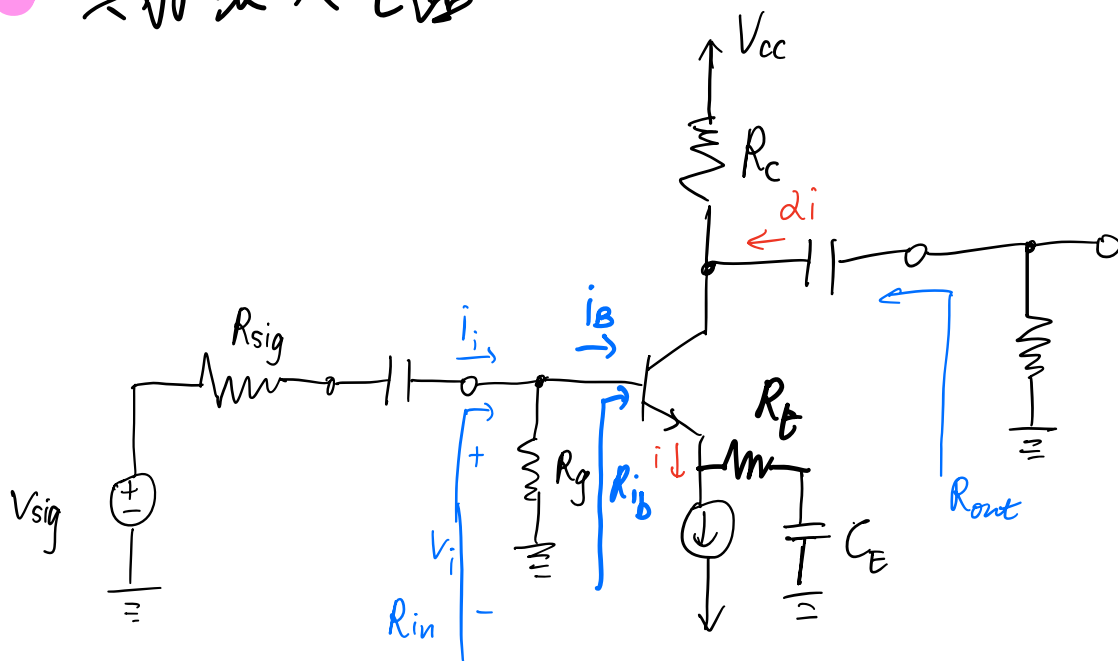

0 C

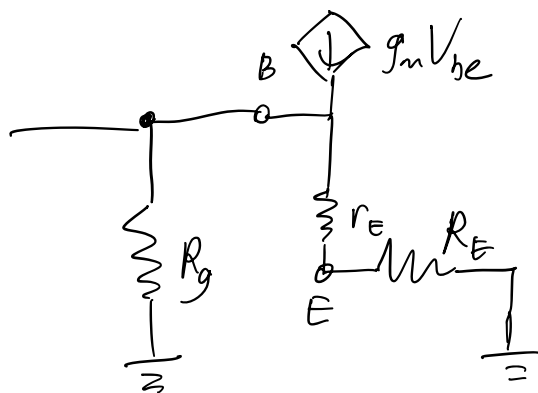

$$R_{in} = \frac{V_i}{i_i} = R_B \parallel R_{ib}$$


$$R_{ib} = \frac{V_i}{i_b} = \frac{(1+\beta)(r_E + R_E)}{1}$$

↓ 流过 r_E 的电流为 $i_E = (1+\beta)i_B$

$$A_v = \frac{V_o}{V_i} = \frac{-\alpha i_c (R_C \parallel R_L)}{i_b (r_E + R_E)} = -\alpha \frac{R_C \parallel R_L}{r_E + R_E}$$

● 集成电路

The Basic BJT Current Mirror

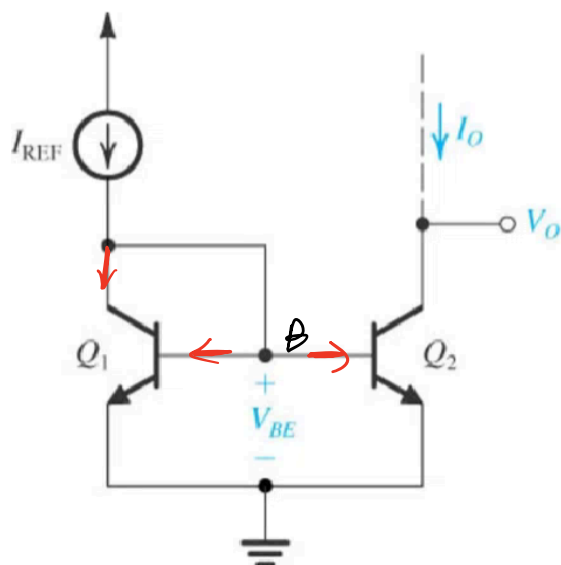

$$I_o = \frac{\beta}{\beta+1} I_E$$


$$I_{REF} = \frac{\beta+2}{\beta+1} I_E$$

$$\frac{I_o}{I_{REF}} = \frac{\beta}{\beta+2} = \frac{1}{1+\frac{2}{\beta}}$$

$$I_{REF} = I_{C1} + I_{B1} + I_{B2}.$$

$$Q_1, Q_2 \text{ 完全相同 } \Rightarrow I_{B1} = I_{B2} = \hat{I}_B, I_{C1} = I_{C2} = \beta \hat{I}_B$$

$$\hat{I}_O \approx \hat{I}_{REF}$$

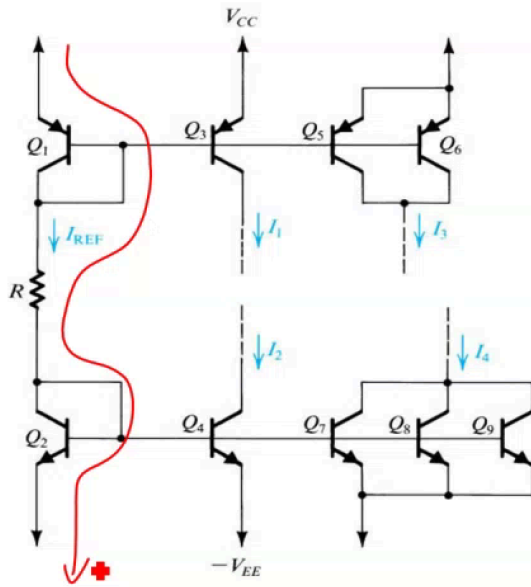

$$I_{REF} = \frac{V_{CC} + V_{EE} - V_{EB1} - V_{BE2}}{R}$$

$$I_1 = I_{REF}$$

$$I_2 = I_{REF}$$

$$I_3 = 2I_{REF}$$

$$I_4 = 3I_{REF}$$

$$- \swarrow \searrow \times m \Rightarrow \bar{I}_m = m I_{REF}$$