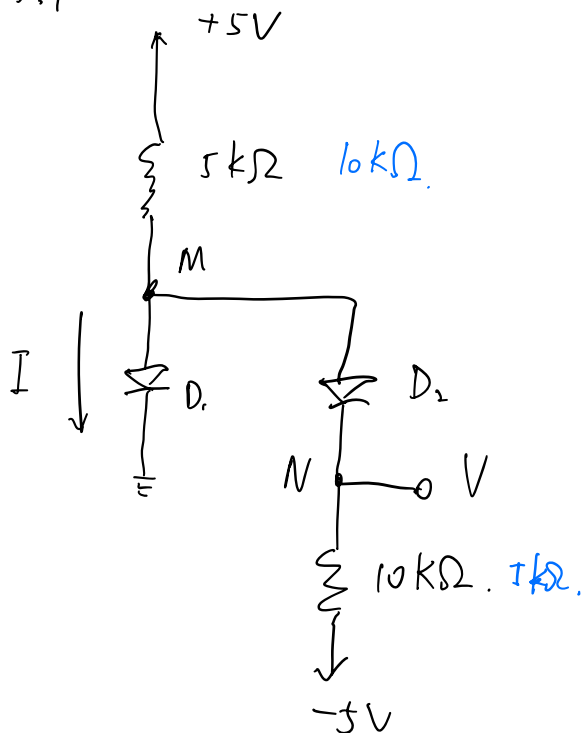


3.9



∴ D_1, D_2 都导通.

$$V_M = 0V. \quad I_1 = \frac{V_0 - V_M}{R_1} = 1mA$$

$$V_N = V_M = 0V. \quad I_2 = \frac{V_N - V_2}{R_2} = 0.5mA$$

$$I_2 < I_1$$

故假设成立, $V = 0V$


(b) ∴ D_1, D_2 都导通

$$V_M = 0V. \quad I_1 = \frac{V_0 - V_M}{R_1} = 0.5mA$$

$$V_N = V = V_M = 0V.$$

$$I_2 = \frac{V_N - V_2}{R_2} = 0.5mA$$

3.23

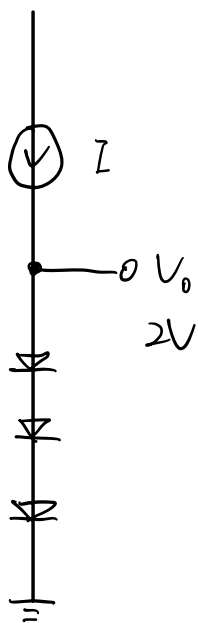

衡量 = 极管与理想模型偏差

$$n=1, \quad I_s = 10^{-14}A$$

$$i = I_s \left(e^{\frac{V}{nV_T}} - 1 \right)$$

$$V_T = 25mV$$

$$\approx I_s e^{\frac{V}{nV_T}}$$

∴ 流过每个二极管电流相同

$$\therefore V_0 = V_{D1} + V_{D2} + V_{D3} = 3V_D = 2V \Rightarrow V_D = \frac{2}{3}V$$

$$I = I_D = 10^{-14} \cdot e^{\frac{V_0}{nV_T}} \approx 3.82mA$$

二极管初始电流为 3.82mA

$$I_D' = I_s e^{\frac{V_0'}{V_T}} \Rightarrow V_T \ln \left(\frac{I_D'}{I_s} \right) = V_0'$$

$$V_0' = 0.025 \ln \left(\frac{2.82 \times 10^{-3}}{10^{-14}} \right) \approx 0.659V$$

$$V_0' = 3V_D' \approx 1.977V \quad \Delta V = -0.023V$$

3.75



$$V_o = 0.7V, \quad I = 1mA$$

$$V_o = 0.1V, \quad I = 1 \times 10^{-6} mA$$

$$V_o = 0.5V, \quad I = 10^{-2} mA$$


$$V_o = 1V, \quad I = 10^3 mA$$

$$V_o = 2V, \quad I = 10^{13} mA$$

$$V_o = 5V, \quad I = 10^{43} mA$$

$$V_o = 10V, \quad I = 10^{93} mA$$

4.37

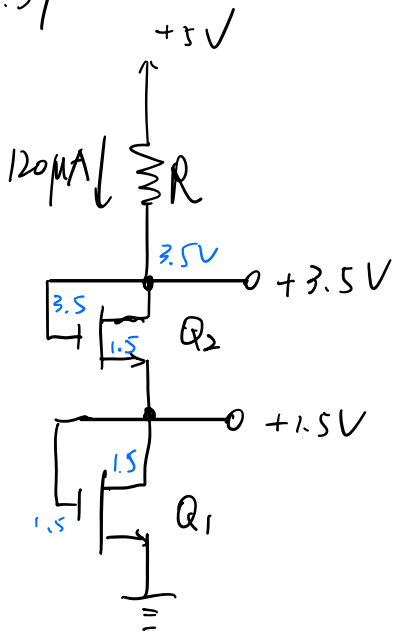

$$V_t = 1V \quad \mu_n C_{ox} = 120 \mu A/V^2$$

$$\lambda = 0 \quad L_1 = L_2 = 1 \mu m$$

$$R = \frac{5V - 3.5V}{120 \mu A} = 12.5 k\Omega$$

对 1.

$$V_{GS} = 2V, V_{DS} = 2.5V. V_{DS} > V_{GS} - V_t$$

→ 在饱和区

$$\text{对 2. } V_{GS} = 1.5V \quad V_{DS} > V_{GS} - V_t$$

→ 在饱和区.

$$I_{D1} = \frac{1}{2} K_n' \frac{W_1}{L} (V_{GS1} - V_t)^2$$

$$= 60 W_1 = 120 \mu A ?$$

$$I_{D2} = \frac{1}{2} K_n' \frac{W_2}{L} (V_{GS2} - V_t)^2$$

$$= 15 W_2 = 120 \mu A ?$$

$$W_1 = 2 \mu m \quad W_2 = 8 \mu m$$

4.42 .

(a) . $V_G = 0V$ $V_S = -10V$.

I_D 在饱和区: $I_D = \frac{1}{2} k'_n/L (V_{GS} - V_t)^2 = I_S$

$\Rightarrow V_{GS} = 4V$. $V_2 = 10V - 4kV \cdot 2mA = 2V$.

$V_1 = -4V$. $\Rightarrow V_{DS} = 6V$ $V_{DS} > V_{GS} \Rightarrow$ 假设成立


(b) $V_G = V_D = V_3$ $V_S = 0$

I_D 在饱和区 $I_D = \frac{1}{2} k'_n/L (V_{GS} - V_t)^2 = 1mA$

$V_{GS} = 3.41V = V_3$.

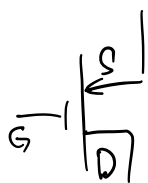(c) $I_D = 2mA = \frac{1}{2} k'_n/L (V_{GS} - V_t)^2$

$\Rightarrow V_{GS} = -4V \Rightarrow V_4 = V_S = 4V$




$V_S = -10V + 2.5k\Omega \cdot 2mA = -5V$

$V_{DS} = -9V$. $V_{DS} < V_{GS} ?$

(d) $I_D = 2mA \Rightarrow V_{GS} = -4V \Rightarrow V_6 = 6V$.

$V_7 = V_6 - 4V = 2V$

4.75 $|V_t| = 0.9V$, $V_A = 50V$, $V_D = 2V$.

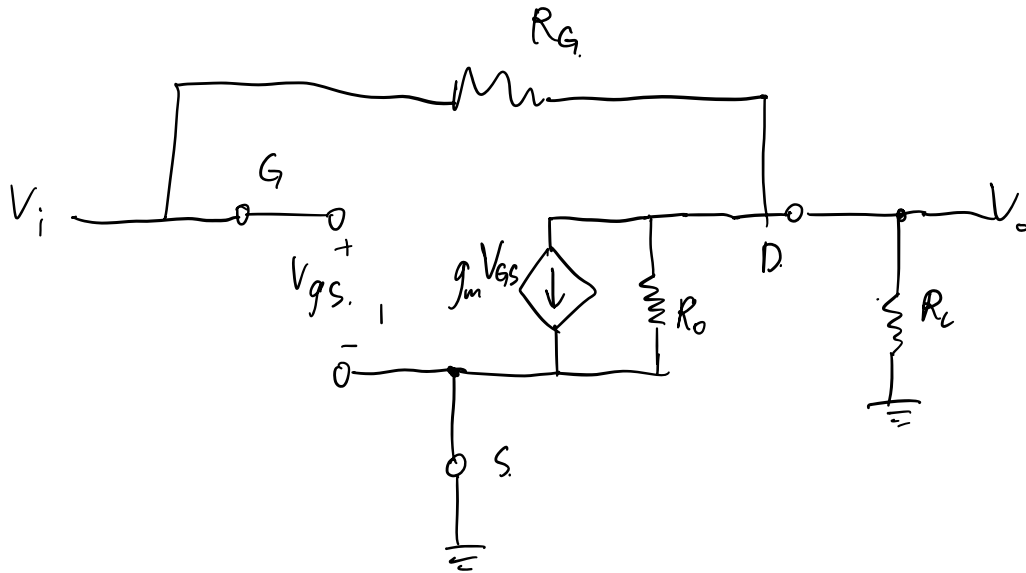


$$R_0 = \frac{V_A}{I_D} = 100k\Omega.$$

$$g_m = k'_n \frac{W}{L} (V_{GS} - V_t)$$

$$= \frac{2I_D}{V_{GS} - V_t} = \frac{2 \cdot 0.5}{2 - 0.9} = 0.91mA/V$$
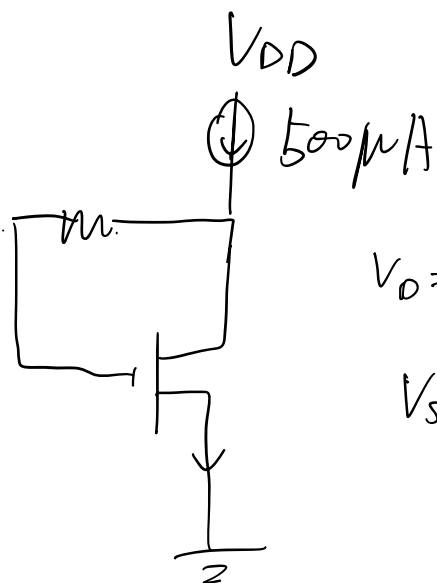
$$\frac{V_o}{V_i} = \frac{-g_m V_{GS} (R_0 // R_L)}{V_{GS}} = -g_m (R_0 // R_L) = -8.3$$



$$V_O = 2V. \quad I_D = 500 \mu A = 0.5 \text{ mA}$$

$$V_S = 0 \quad V_{DS1} = 2V = V_{GS1}$$

$$I_{D1} = \frac{1}{2} \mu_n \frac{W}{L} (V_{GS1} - V_t)^2 = 0.5 \text{ mA}$$

$$I_{D2} = 1 \text{ mA}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{2}{1} = \frac{(V_{GS2} - V_t)^2}{(V_{GS1} - V_t)^2}$$

$$V_{GS2} = 0.9 + \sqrt{2}(2 - 0.9) = 2.5 \text{ V}$$

$$V_O = 2.5 \text{ V}$$


修改后:

$$g_{m2} = 1.3 \text{ mA/V}$$

$$r_{o2} = \frac{V_A}{I_D} = 50 \text{ k}\Omega$$

$$A = -g_{m2} (r_{o2} \parallel R_L) = -10.8$$

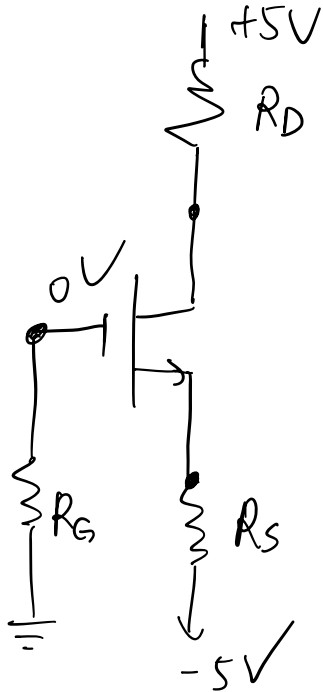4.87 $V_t = 1V$, $K_n' W/L = 0.8 \text{ mA/V}^2$ $V_A = 40V$



(a) $I_D = 0.1 \text{ mA}$

$$= \frac{1}{2} \cdot 0.8 \cdot (V_{GS} - V_t)^2$$

$$\Rightarrow V_{GS} = 1.5V \quad V_G = 0V$$

$$V_S = -5V + I_D R_S = -1.5V$$

$$R_S = 35 \text{ k}\Omega$$

$$V_G = (V_{GS} - V_t) + V_t + V_S = 0V$$

$$R_D = \frac{5 - 0}{0.1} = 50 \text{ k}\Omega$$


$$R_G = 10 \text{ M}\Omega$$

(b) $g_m = \frac{2I_D}{V_{GS} - V_t} = 0.4 \text{ mA/V}$

$$r_o = \frac{V_A}{I_D} = 400 \text{ k}\Omega$$

(c)



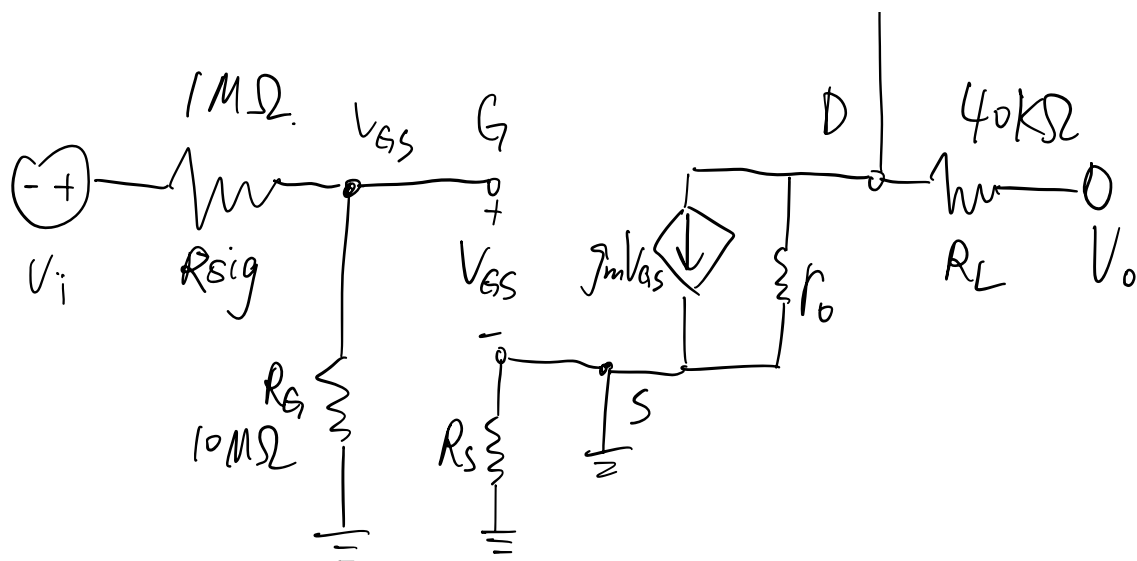

$$V_o = -g_m V_{GS} \left((r_o \parallel R_D) + 40 \right)$$

$$V_i = \frac{V_{GS}}{R_G} (R_G + R_{sig})$$

$$\frac{V_o}{V_i} =$$

(d) 模型

$$CD: A_{v_o} = \frac{r_o \parallel R_S}{\frac{1}{g_m} + (r_o \parallel R_S)} = 0.93$$

$$R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_S = 2.3 k\Omega$$

$$(c) R_{in} = \frac{1}{g_m} \parallel R_S = 2.33 k\Omega$$

$$\hat{i}_i = i_{sig} \frac{R_{sig}}{R_{sig} \parallel R_{in}} = 9.77 mA$$

$$\hat{i} = \frac{R_S}{R_S + \frac{1}{g_m}} \hat{i}_i = 9.12 mA$$

$$V_g = R_D \cdot \hat{i} = 0.46 V$$

5.80

$$(a) I_E = 2 mA \quad I_B = \frac{1}{\beta+1} I_E = 0.0198 mA$$

$$I_C = \frac{\beta}{\beta+1} I_E = 1.98 mA$$

$$V_B = -I_B \cdot R_B \quad V_1 = V_B - V_{BE} = -1.136 V$$

$$V_2 = 5V - I_C R_C = 1.832 V$$

$$(b) \quad V_B = 0V, \quad V_E = -0.7V \quad \bar{I}_4 = \frac{V_E - (-5V)}{2.2k\Omega} \\ = 1.955mA$$

$$\bar{I}_C = \frac{\beta}{\beta+1} \bar{I}_4 \Rightarrow V_3 = 5 - 1.6 \cdot \frac{100}{101} \bar{I}_4 \\ = 1.904V$$

$$(c) \quad 0 - \frac{\bar{I}_E}{1+\beta} \cdot 22 - 0.7 - 2.2 \bar{I}_E = -5$$

$$\Rightarrow \bar{I}_E = 1.778mA$$

$$V_7 = 5 - \frac{\beta}{1+\beta} \bar{I}_E \times 1.6 = 2.183V$$

$$V_5 = -5 + 2.2 \bar{I}_E = -1.087V$$

$$V_6 = V_5 + 0.7 = -0.387V$$

$$(d) \quad 5 - 3.3\bar{I}_E - 0.7 - \frac{1}{\beta+1} \bar{I}_E \cdot 56 = 1.2$$

$$\Rightarrow \bar{I}_E = 0.8147 \text{ mA}$$

$$V_A = 5 - 3.3\bar{I}_E = 2.3164 \text{ V}$$

$$\begin{aligned} V_Q &= -5 \text{ V} + 5.1 \cdot \frac{\beta}{\beta+1} \cdot \bar{I}_E \\ &= -0.8862 \text{ V} \end{aligned}$$

$$(e) \quad V_{BB} = -5 + \frac{150}{150+91} \cdot (5+5) = 1.224 \text{ V}$$

$$R_{BB} = (150 // 91) = 56.64 \text{ k}\Omega$$

$$5 - 3.3\bar{I}_E - 0.7 - \frac{\bar{I}_E}{\beta+1} R_{BB} = 1.224 \text{ V}$$

$$\Rightarrow \bar{I}_E = 0.7967 \text{ mA}$$

$$V_{I1} = 5 - 3.3\bar{I}_E = 2.371 \text{ V}$$

$$V_{12} = \frac{\beta}{\beta+1} \bar{I}_E \cdot 5 - 1 - 5 = 0.977V$$

$$V_{10} = V_{11} - 0.7V$$


5.130.

$$V_{BB} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

$$R_B = (R_1 // R_2) = 9.64k\Omega$$

$$V_{BB} - \frac{1}{\beta+1} \bar{I}_E R_B - 0.7 - \bar{I}_E R_E = 0$$

$$\Rightarrow \bar{I}_E = 1.94mA$$

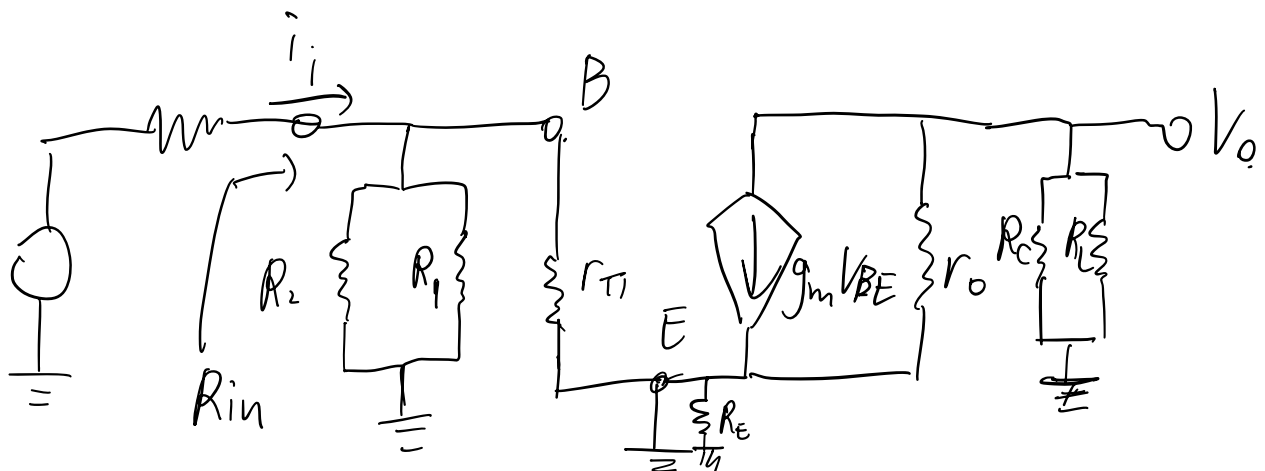

$$V_o = -g_m V_{\pi} (R_C // R_L)$$

$$\hat{i}_i = \frac{V_{\pi}}{(R_1 // R_2 // R_{\pi})}$$

$$\begin{aligned} V_{sig} &= V_{\pi} + \hat{i}_i R_{sig} \\ &= \left(1 + \frac{R_{sig}}{R_1 // R_2 // R_{\pi}}\right) V_{\pi} \end{aligned}$$

$$\frac{V_o}{V_{sig}} = \frac{-g_m (R_c // R_L)}{1 + \frac{R_{sig}}{(R_1 // R_2 // R_{\pi})}} = -8.13$$

$$\hat{i}_o = \frac{V_o}{R_L} = -g_m V_{\pi} \frac{(R_c // R_L)}{R_L}$$

$$\frac{\hat{i}_o}{\hat{i}_i} = \frac{-g_m \frac{(R_c // R_L)}{R_L}}{(R_1 // R_2 // R_{\pi})} = -45.3$$

$$g_m = I_C / V_T \quad r_{\pi} = \beta / g_m \quad r_o = \frac{V_A}{I_C}$$

5.136.


$$I_E = 0.1 \text{ mA}, \quad I_B = \frac{1}{\beta+1} I_E$$

$$= 9.9 \times 10^{-4} \text{ mA}$$

$$I_C = 9.9 \times 10^{-2} \text{ mA}$$

$$g_m = I_C / V_T = 1.41 \times 10^{-3} \text{ mA/V}$$
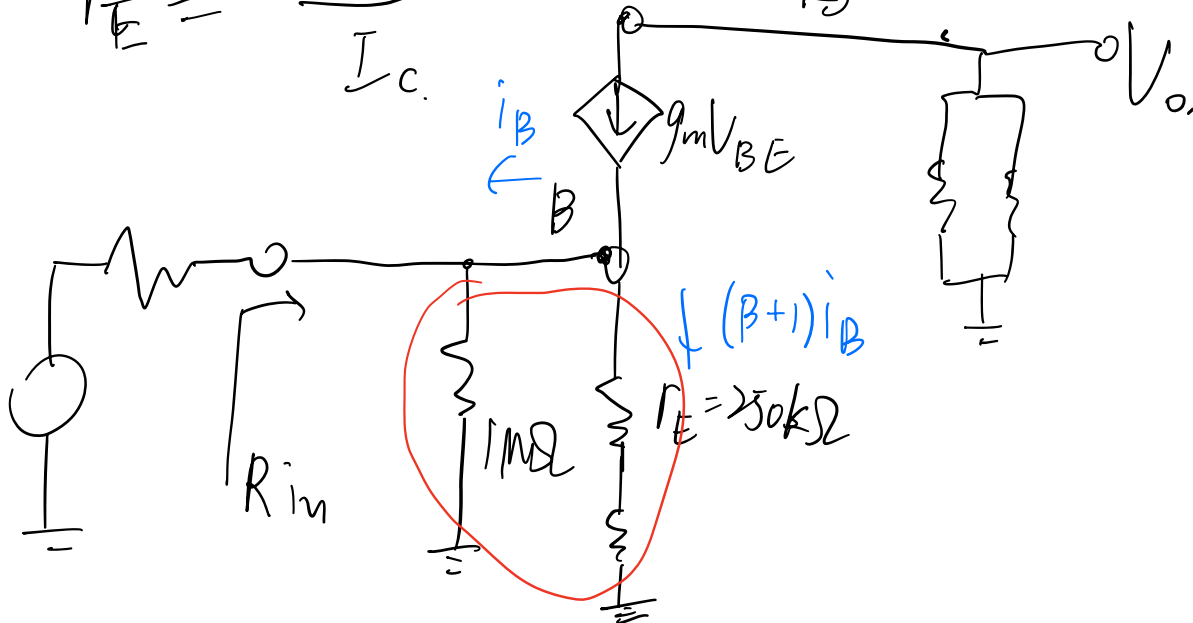
$$r_E = \frac{\frac{\beta}{1+\beta}}{I_C} = 250 \Omega$$



$$R_{in} = 50.5 k\Omega$$

$$\frac{U_b}{U_s} = \frac{R_{in}}{R_s + R_{in}} = 0.72$$

$$\frac{U_o}{U_b} = \frac{-\beta (r_o || r_o)}{(r_e + R_E)} = -19.8$$

$$U_{be} = 5mV, U_e = 5mV$$

$$U_b = 10mV \quad U_s = 13.88mV$$

$$U_o = 13.88 \times 14.2$$

$$= 197.2mV$$

5.147

(a).

$$V_{BB} = 4.5V. \quad R_{BB} = 10k\Omega.$$

$$4.5 - \frac{1}{\beta+1} \bar{I}_E (10+10) - 0.7 -$$

$$2 \bar{I}_E = 0.$$

$$\Rightarrow \bar{I}_E = 1.73 \text{ mA}$$


$$I_C = 1.71 \text{ mA}.$$

$$g_m = \frac{I_C}{V_T} = 68.5 \text{ mA/V}$$

$$r_e = \frac{\frac{\beta}{\beta+1}}{g_m} = 14.5k\Omega$$

$$r_{\pi} = \frac{\beta}{g_m} = 1.46k\Omega.$$

(b).

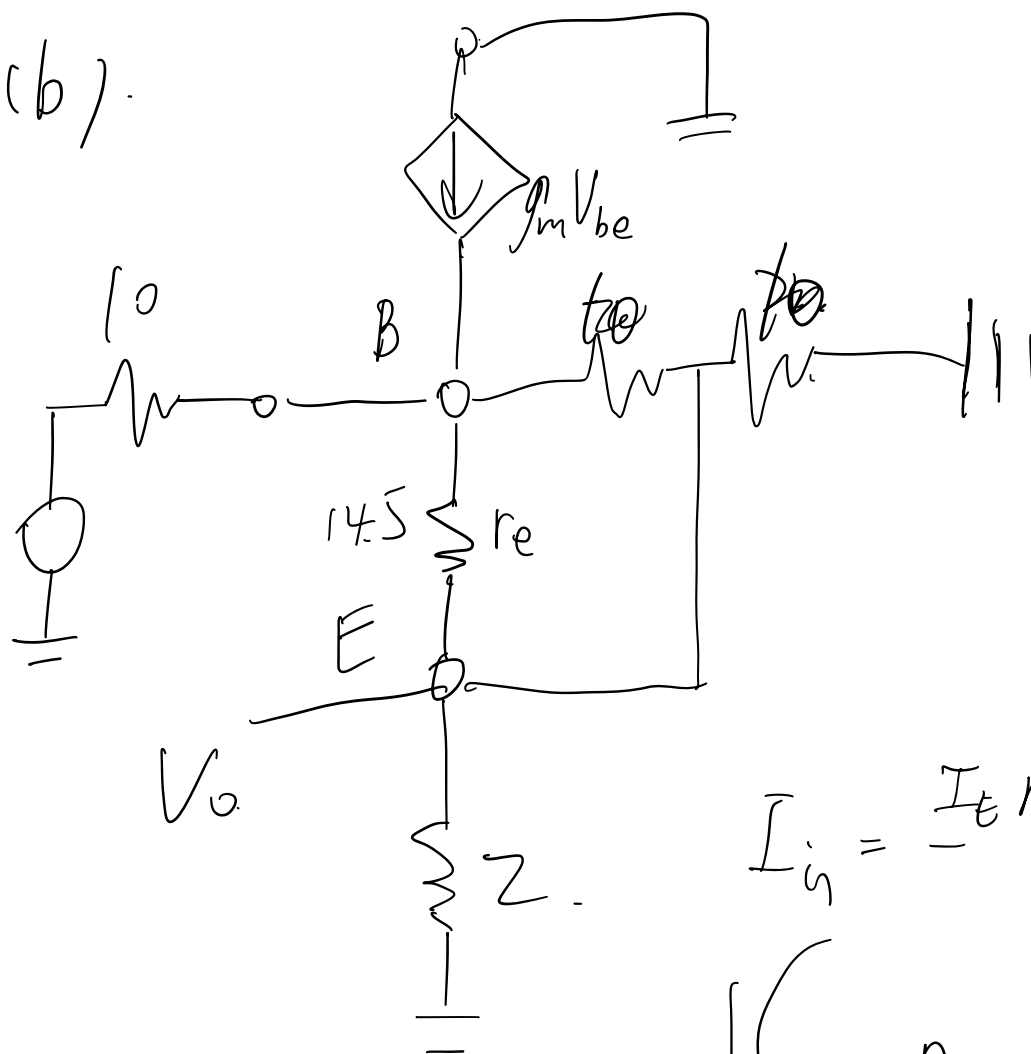

$$I_{in} = I_E r_e \left(\frac{1}{r_e} + \frac{1}{\omega} \right)$$

$$V_o = (2 // \omega) \cdot I_E$$

$$R_i = \frac{U_b}{I_{in}} = \frac{U_b}{I_E r_e \left(\frac{1}{r_e} + \frac{1}{\omega} \right)} = \frac{r_e}{1 + \omega r_e}$$

$$\frac{V_o}{V_{sig}} = \frac{U_b}{V_{sig}} \cdot \frac{V_o}{U_b} =$$

$$\frac{R_i}{R_i + R_s} = \frac{114.48}{115.48} = 0.92.$$

6.34, $\beta = \infty \Rightarrow \hat{i}_B = 0, \hat{i}_E = \hat{i}_C$

6.34 Find the voltages at all nodes and the currents through all branches in the circuit of Fig. P6.34. Assume $|V_{BE}| = 0.7$ V and $\beta = \infty$.

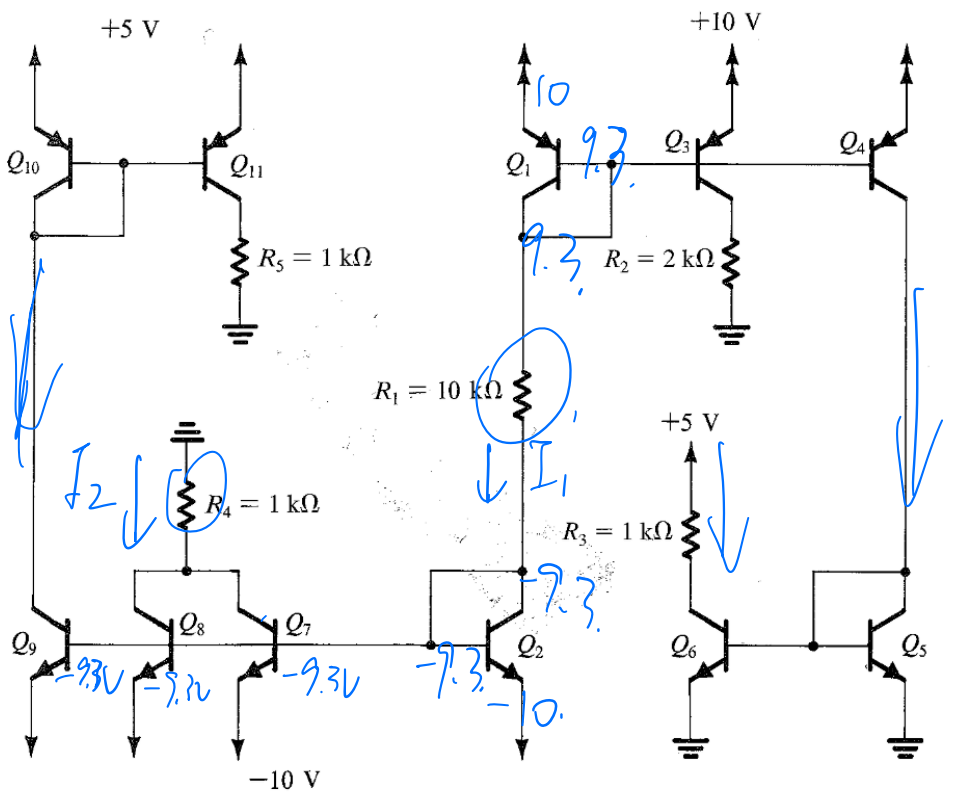


FIGURE P6.34

$$I_i = \frac{2 \times 9.3}{R_i} = 1.86 \text{ mA}$$

$$I_{c1} = I_{c2} = \dots = I_{c6} =$$

$$= I_{c11} = 1.86 \text{ mA}$$

$$V_{c3} = 3.72 \text{ V}$$

$$V_{c6} = 3.14 \text{ V}$$


$$V_{c11} = 1.86 \text{ V}$$

$$V_{c5} = 0.7 \text{ V}$$

$$V_{c7} = -3.72 \text{ V}$$


2.8

(a)

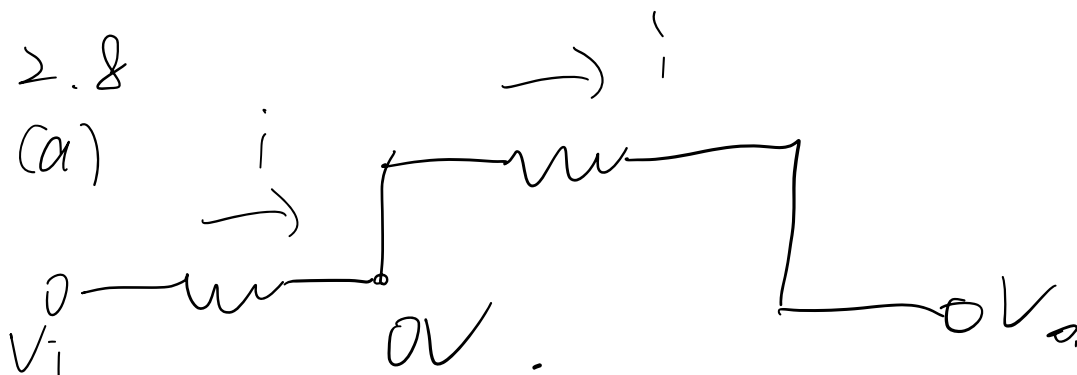

$$\frac{V_o}{V_i} = \frac{100}{-10} = -10. \quad R_{in} = 10k\Omega$$

(b)

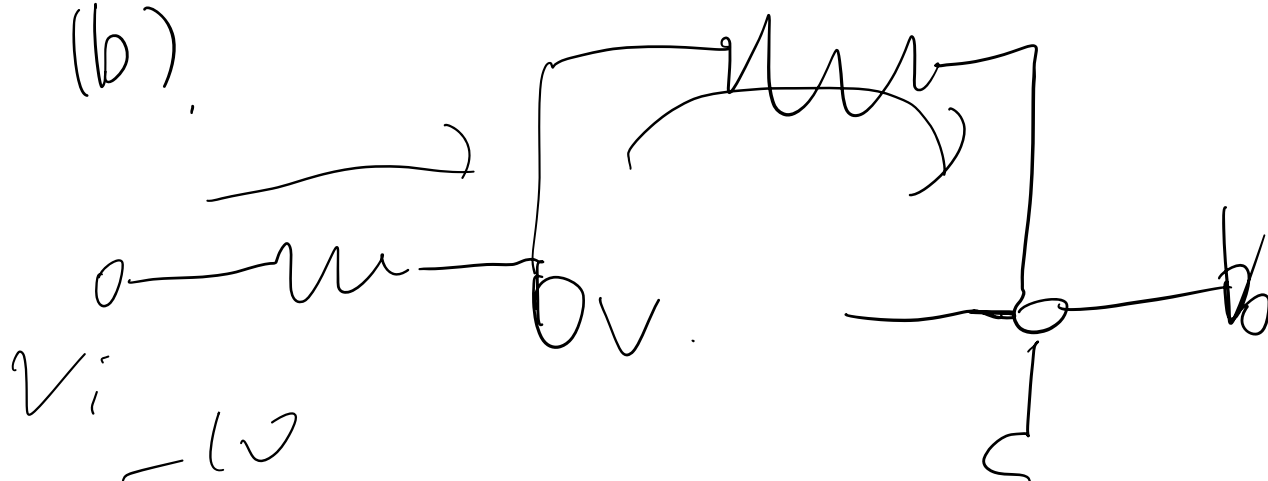

$$\frac{V_o}{V_i} = \frac{100}{-10} = -10. \quad \underline{0V}$$

$$R_{in} = 10k\Omega$$

$$(c) \quad \frac{U_o}{U_i} = -10, \quad R_{in} = 20$$

$$(d), \quad \frac{U_o}{U_i} = -10, \quad R_{in} = 10$$

2.50.

~~叠加~~ 原理

$$V_{o1} = -20V_1$$

$$V_{o2} = V_2 \left(\frac{20R}{21R} \right)$$





$$V_{02} = V_2 \left(\frac{R_L}{R} \right) \left(\frac{R}{R+R_L} \right)$$

$$= 20V_2$$

$$V_0 = V_{01} + V_{02}$$

$$= 4 \sin(2\pi \times 1000 t)$$

2. b2.

$$V_1 \text{ only: } R_I = \frac{U_1}{I} = R.$$

$$V_2 \text{ only: } R_I = 2R.$$

?? between 2 terminals

$$R_I = \frac{U}{I} = 2R.$$

$$V_+ = V_- = 0.$$

?? V_s connected to both V_1 and V_2 .

$$R_I = \frac{U}{I} = R. \quad V_+ = V_- = \frac{U_2}{2}$$

13.26.

13.26 For the circuit in Fig. P13.26, sketch and label the transfer characteristic v_o-v_I . The diodes are assumed to have a constant 0.7-V drop when conducting, and the op amp saturates at ± 12 V. What is the maximum diode current?

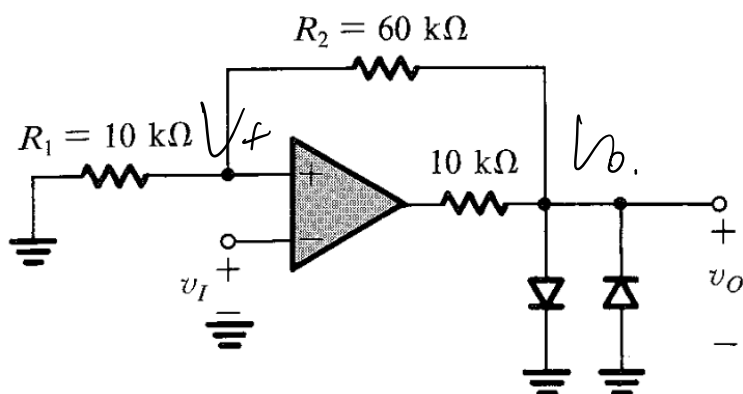


FIGURE P13.26

$$V_+ = \frac{1}{7} V_o$$

$$V_o = 0.7 \text{ V} / -0.7 \text{ V}$$

$$V_+ = 0.1 \text{ V} / -0.1 \text{ V}$$

